


## Alternating Current (AC) Circuits

- We have been talking about DC circuits
  - Constant currents and voltages
  - Resistors
  - Linear equations
  
- Now we introduce AC circuits
  - Time-varying currents and voltages
  - Resistors, capacitors, inductors (coils)
  - Linear *differential* equations

65

Recall water analogy for Ohm's law...


- (a) Battery  
(b) Resistor

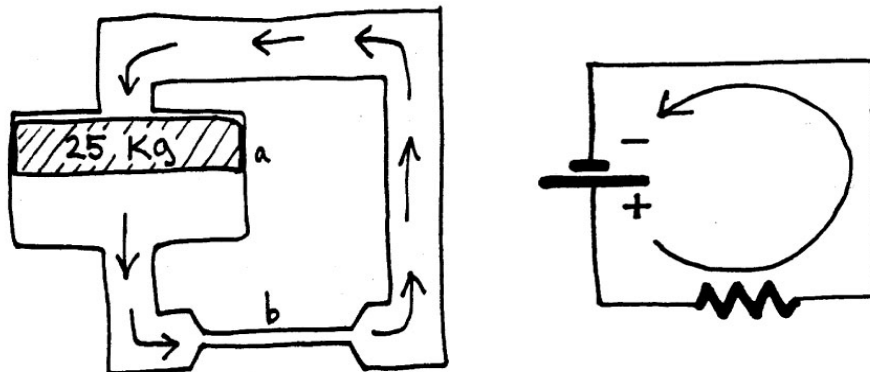

66

Now we add a steel tank with rubber sheet

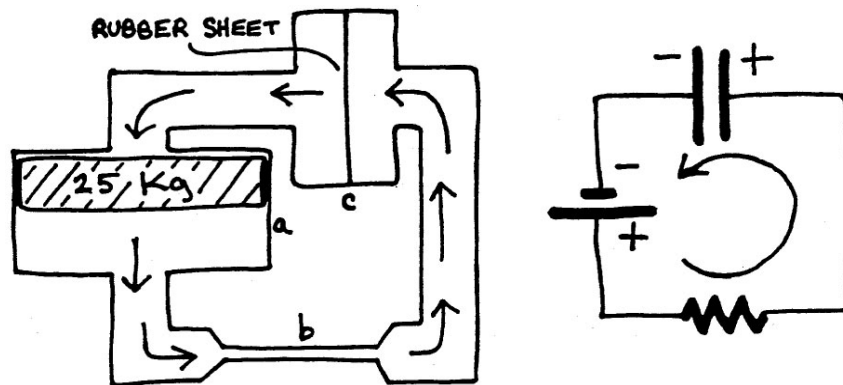- (a) Battery
- (b) Resistor
- (c) *Capacitor*




67

Water enters one side of the tank and leaves the other, distending but not crossing the sheet.


How to decrease *capacitance* of tank?

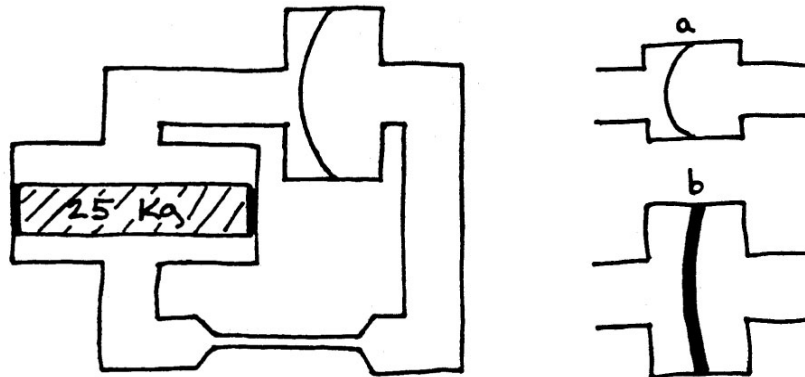Make rubber sheet (a) smaller or (b) thicker,  
(or use stiffer rubber).




68

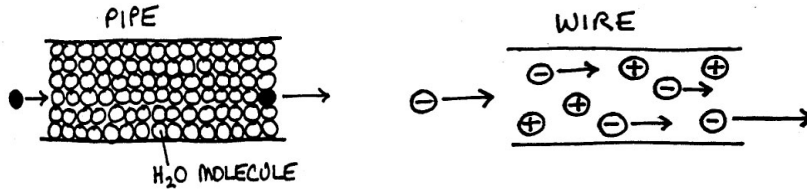Charge, like water is practically incompressible,



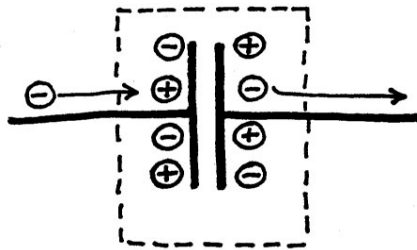but within a small volume (closely spaced plates) charge can enter one side and leave the other, without flowing across the space between.




69

### Basic Laws of Capacitance

- Capacitance  $C$  relates charge  $Q$  to voltage  $V$


$$C = \frac{Q}{V}$$

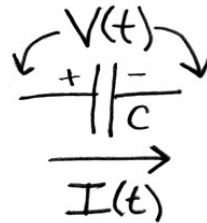

- Since  $Q = \int I dt$ ,

$$V = \frac{1}{C} \int I dt$$

$$I = C \frac{dV}{dt}$$

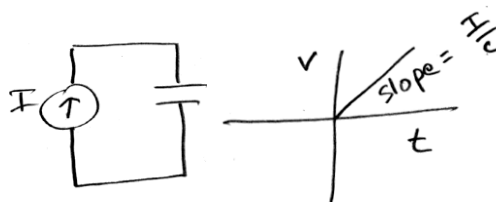

- Inductance has units of *Farads*, F.

70

## Charging a Capacitor with Battery $V_B$

- Voltage across resistor to find current

$$I(t) = \frac{V_B - V(t)}{R}$$


- Basic law of capacitor

$$I(t) = C \frac{dV_C(t)}{dt}$$


- Differential Equation yields exponential

$$V_C(t) + RC \frac{dV_C(t)}{dt} = V_B$$
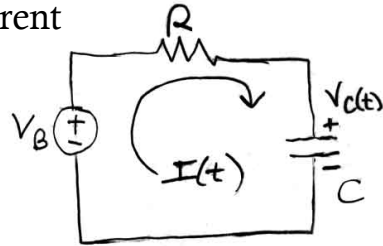
$$V_C(t) = V_B \left( 1 - e^{-\frac{t}{RC}} \right)$$



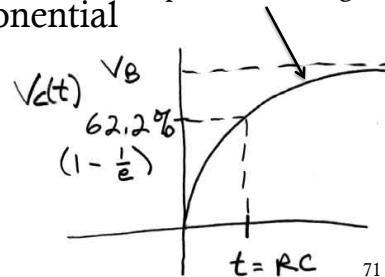diminishing returns as cap becomes charged




71

## What determines *capacitance C*?

- Area  $A$  of the plates
- Distance  $d$  between the plates
- Permittivity*  $\epsilon$  of the *dielectric* between plates.

$$C = \epsilon \frac{A}{d}$$

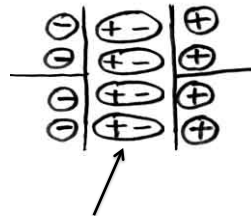

Alignment of dipoles within *dielectric* between plates increases capacitor's ability to store charge (capacitance).


*Permittivity* of a vacuum  $\epsilon_0 \approx 8.8541 \times 10^{-12} \text{ F} \cdot \text{m}^{-1}$ .

72
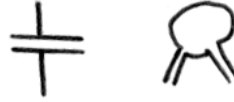
## Types of Capacitors


- Disk (Ceramic) Capacitor

- Non-polarized
- Low leakage
- High breakdown voltage
- $\sim 5\text{pF} - 0.1\ \mu\text{F}$



- Electrolytic Capacitor

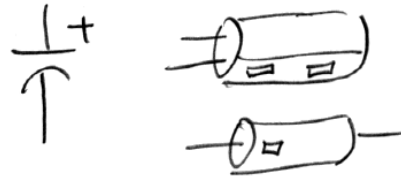- High leakage
- Polarized
- Low breakdown voltage
- $\sim 0.1\ \mu\text{F} - 10,000\ \mu\text{F}$





- Supercapacitor (Electrochemical Double Layer)

- New. Effective spacing between plates in nanometers.
- Many Farads! May power cars someday.

73

## Inductor (coil)

- Water Analogy

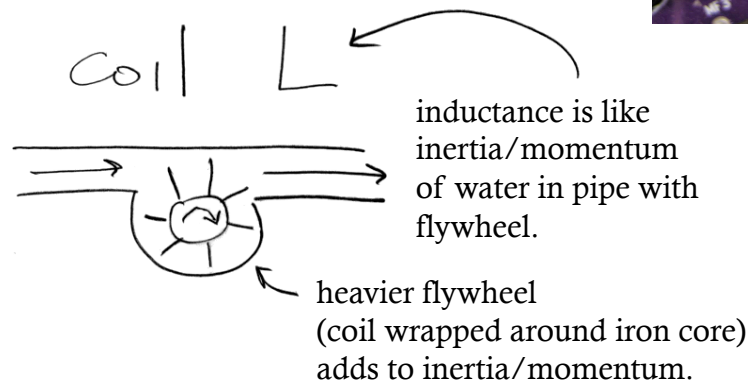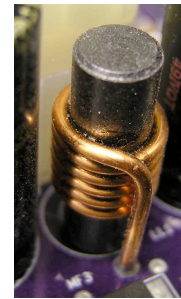


74

## Basic Laws of Inductance

- *Inductance*  $L$  relates changes in the current to voltages induced by changes in the magnetic field produced by the current.

$$I = \frac{1}{L} \int V dt$$

$$V = L \frac{dI}{dt}$$

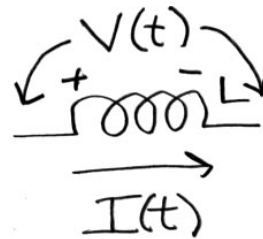


- Inductance has units of *Henries*, H.

75
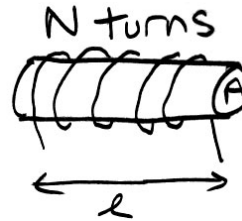
## What determines *inductance* $L$ ?

- Assume a solenoid (coil)
- Area  $A$  of the coil
- Number of turns  $N$
- Length  $\ell$  of the coil
- *Permeability*  $\mu$  of the core



$$L = \mu \frac{N^2 A}{\ell}$$

*Permeability* of a vacuum  $\mu_0 \approx 1.2566 \times 10^{-6} \text{ H} \cdot \text{m}^{-1}$ .

76

## Energy Stored in Caps and Coils

- Capacitors store “potential” energy in electric field

$$E = \frac{1}{2} CV^2 \quad \text{independent of history}$$

- Inductors store “kinetic” energy in magnetic field

$$E = \frac{1}{2} L I^2 \quad \text{independent of history}$$

- Resistors don't store energy at all!

error in Scherz Eq. 2.42: missing “dt”


77

## What is Magnetism?

- Lorentz Contraction  $l = l_0 \sqrt{1 - v^2/c^2}$

Length  $l$  of object observed in relative motion to the object is shorter than the object's length  $l_0$  in its own rest frame as velocity  $v$  approaches speed of light  $c$ .

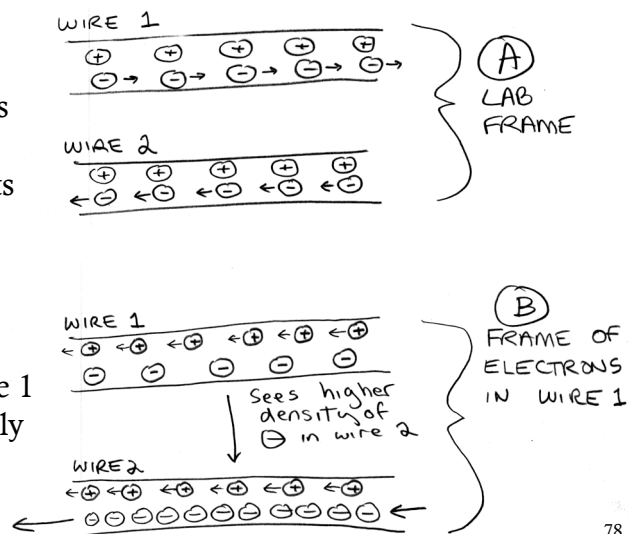
Thus electrons in Wire 1 see Wire 2 as negatively charged and repel it:  
Magnetism!



78

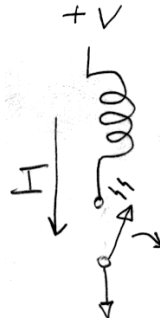
## Generating Sparks

- What if you suddenly try to stop a current?



$$V = L \frac{dI}{dt}$$

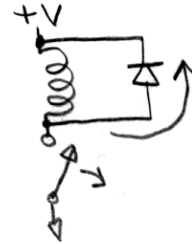goes to  $-\infty$  when  
switch is opened.



use diode to shunt  
current, protect switch.

- Nothing changes instantly in Nature.
- Spark coil used in early radio (Titanic).
- Tesla patented the spark plug.

79

## Symmetry of Electromagnetism



$$I = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int I dt$$



$$V = L \frac{dI}{dt}$$

$$I = \frac{1}{L} \int V dt$$

- Only difference is no magnetic monopole.

80


## Inductance adds like Resistance

parallel



$$L_P = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

series

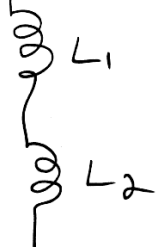

$$L_S = L_1 + L_2$$

81


## Capacitance adds like Conductance

parallel



$$C_P = C_1 + C_2$$

series

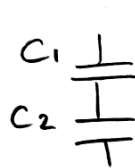

$$C_S = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$$

82