

## Trigonometry Revealed

remember the end of trig?

$$\sin 2t = 2 \sin t \cos t$$

$$\cos 2t = \cos^2 t - \sin^2 t$$

$$\sin \frac{1}{2} t = \pm \sqrt{\frac{1}{2}(1 - \cos t)}$$

you had to take them  
on faith, ...  
No longer!


108

Now you can prove them

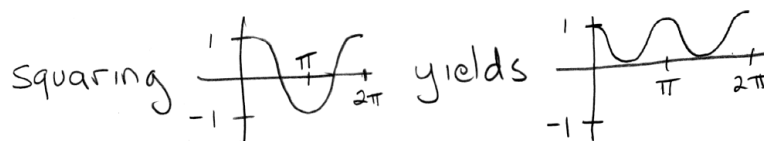example

$$\cos^2 \theta = \frac{1 + \cos 2\theta}{2}$$


$$\begin{aligned} \left( \frac{e^{j\theta} + e^{-j\theta}}{2} \right)^2 &= \frac{e^{j2\theta} + e^{-j2\theta} + e^0 + e^0}{4} \\ &= \frac{\cos 2\theta}{2} + \frac{1}{2} \end{aligned}$$



109
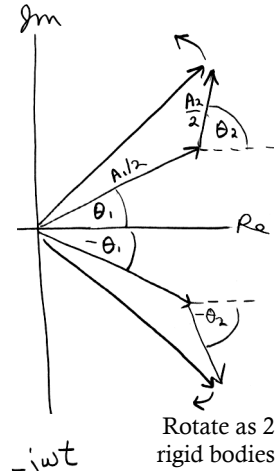
## Superposition Revealed

The forward and backward spinning phasors within two sinusoids at the same frequency group independently.



$A_1 \cos(\omega t + \theta_1) + A_2 \cos(\omega t + \theta_2)$   
 is a sinusoid of frequency  $\omega$

$$\left[ \frac{A_1}{2} e^{j\theta_1} + \frac{A_2}{2} e^{j\theta_2} \right] e^{j\omega t} + \left[ \frac{A_1}{2} e^{-j\theta_1} + \frac{A_2}{2} e^{-j\theta_2} \right] e^{-j\omega t}$$

Single complex number and its complement completely describe its phase and amplitude.


110

## Complex Impedance - Capacitor

Complex impedance  $Z$

replaces resistance  $R$  (which is real)

$$I_c(t) = C \frac{dV_c(t)}{dt}$$

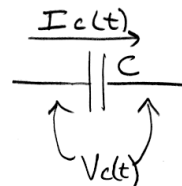

$$\text{if } V_c(t) = e^{j\omega t}$$

$$\text{then } I_c(t) = j\omega C e^{j\omega t}$$

Complex Impedance using Ohms Law

$$Z_c = \frac{V_c(t)}{I_c(t)} = \frac{e^{j\omega t}}{j\omega C e^{j\omega t}} = \boxed{\frac{1}{j\omega C}} = -\frac{j}{\omega C}$$

111

## Complex Impedance - Inductor

Like wise for a coil

$$V_L(t) = L \frac{dI_L(t)}{dt}$$

$$\text{if } I_L(t) = e^{j\omega t}$$

$$\text{then } V_L(t) = j\omega L e^{j\omega t}$$


Complex impedance

$$Z_L = \frac{V_L(t)}{I_L(t)} = \frac{j\omega L e^{j\omega t}}{e^{j\omega t}} = \boxed{j\omega L}$$

112

## Complex Impedance - Resistor

what is complex impedance of resistor

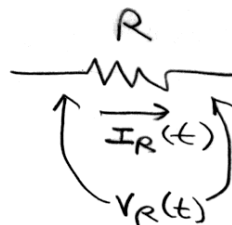


$$V_R(t) = e^{j\omega t}$$

$$I_R(t) = \frac{e^{j\omega t}}{R}$$

$$Z_R = \boxed{R} \quad \text{pure real}$$


113

## Impedance on the Complex Plane

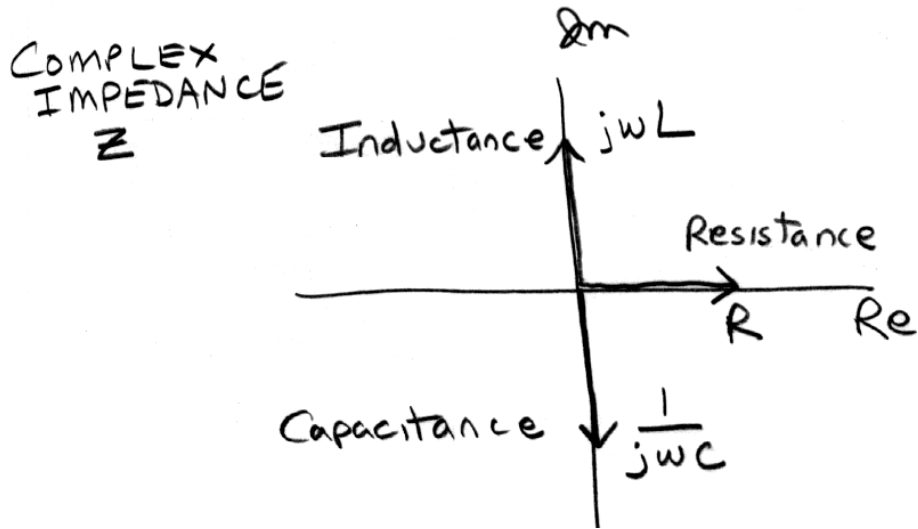

114

## Taxonomy of Impedance

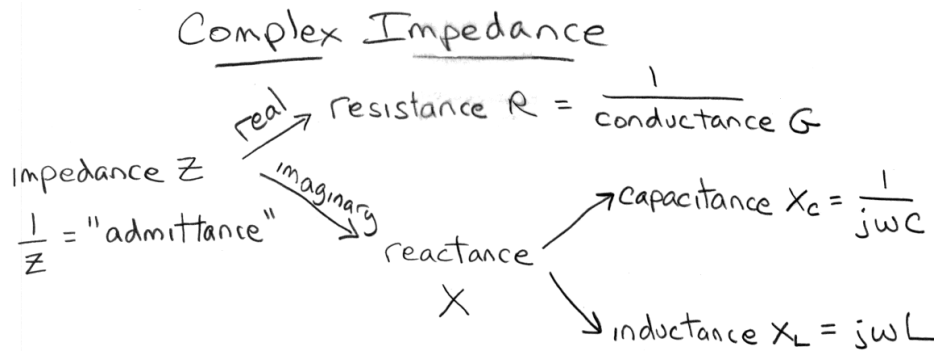


"X" sometimes used if purely imaginary, or just "Z<sub>C</sub>" and "Z<sub>L</sub>"

115

## Series Capacitors and Inductors

Two capacitors in series:

Series

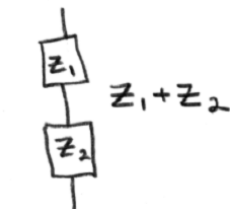

$$Z = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} = \frac{C_1 + C_2}{j\omega C_1 C_2} = \frac{1}{j\omega \left( \frac{1}{C_1} + \frac{1}{C_2} \right)}$$

Two inductors in series:


$$Z = j\omega L_1 + j\omega L_2 = j\omega(L_1 + L_2)$$

116

## Parallel Capacitors and Inductors

Two capacitors in parallel:

Parallel



$$Z = \frac{1}{j\omega C_1 + j\omega C_2} = \frac{1}{j\omega(C_1 + C_2)}$$

Two inductors in parallel:


$$Z = \frac{1}{\frac{1}{j\omega L_1} + \frac{1}{j\omega L_2}} = j\omega \left( \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} \right)$$

117

## Same rules as DC circuits

### THEVENIN EQUIVALENT

ANY NETWORK OF

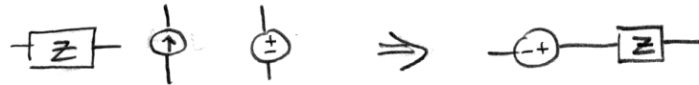


### NORTON EQUIVALENT

ANY NETWORK OF



118
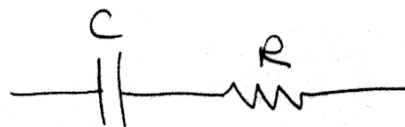
## Impedance of a Passive Branch – RC circuit




$$Z = \frac{1}{j\omega C} + R = \frac{1 + j\omega \overbrace{RC}^{\text{time constant}}}{j\omega C}$$

$$Z = R \quad | \omega \gg \frac{1}{RC} \quad \text{Resistor dominates}$$

$$Z = \frac{1}{j\omega C} \quad | \omega \ll \frac{1}{RC} \quad \text{Capacitor dominates}$$

119


### LC circuit - Resonance

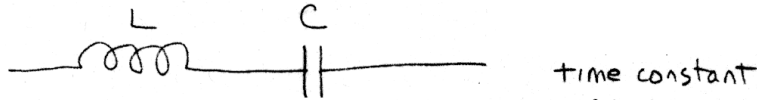

$$Z = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$


$$Z = 0 \quad | \quad \omega = \frac{1}{\sqrt{LC}} \quad \text{Resonance}$$

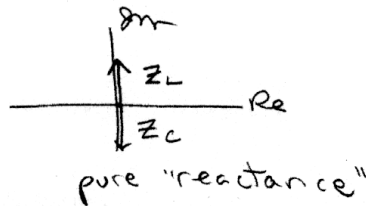At resonance, impedances add to zero and cancel.



Analogous to spring and weight system – Energy is passed between magnetic and electric fields, as in electromagnetic wave.

### Adding R to LC damps the ringing

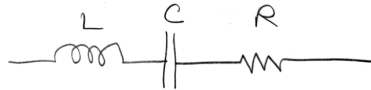


$$Z = j\omega L + \frac{1}{j\omega C} + R =$$

$$\frac{1 - \omega^2 LC}{j\omega C} + R =$$

$$j\left(\frac{\omega^2 LC - 1}{\omega C}\right) + R$$


pure imaginary
pure Real

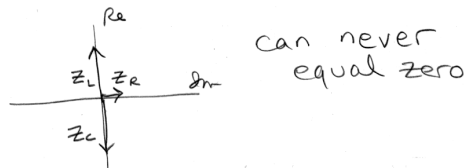

Like dragging your feet on the swing. Energy being passed from magnetic to electric field eventually dissipated by resistor as heat.

## "Tank" Circuit

put coil and cap in loop

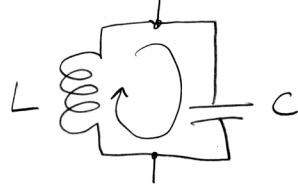

COOL FACT  
speed of light

$$C = \frac{1}{\mu_0 \epsilon_0}$$

"inductance" and  
"capacitance" of  
free space

Current sees no impedance

$$\text{at } \omega = \frac{1}{\sqrt{LC}}$$


will resonate and absorb  
radio frequency (RF) energy

used in anti shoplifting tags.

also pipe organs  
and microwave  
tubes.

122

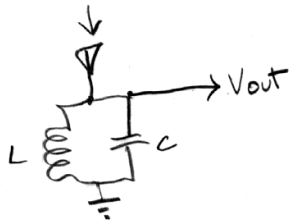"Tank" circuit first thing after  
antenna in radio receiver



$$Z = \frac{1}{\frac{1}{j\omega L} + \frac{1}{j\omega C}} = \frac{1}{j\omega L + j\omega C} =$$

$$\frac{j\omega L}{1 - \omega^2 LC} = \infty \quad \left| \quad \omega = \frac{1}{\sqrt{LC}}\right.$$

- How can impedance be infinite through the parallel LC circuit when each of the components can pass current?
- At the resonant frequency the currents trying to pass from the antenna to ground are shifted 90° in opposite directions and thus are 180° out of phase and cancel.
- This "null point" is an example of how lenses work with light.

123