

1310 Homework 5

① Prove that

$$A_1 \cos(\omega t + \theta_1) + A_2 \cos(\omega t + \theta_2) = A_3 \cos(\omega t + \theta_3)$$

where the phase θ_3 and magnitude A_3 can be expressed as a single complex number


$$(A_1 e^{j\theta_1} + A_2 e^{j\theta_2})$$

② Prove the following trig identities using complex exponentials

$$\sin 2t = 2 \sin t \cos t$$


$$\cos 2t = \cos^2 t - \sin^2 t$$

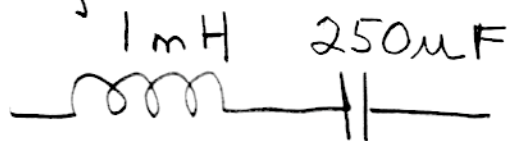③ Write an expression for the complex impedance of the circuit branch below as a function of frequency ω . At what frequency is the impedance 0? (in Hz)




answer: 318 Hz

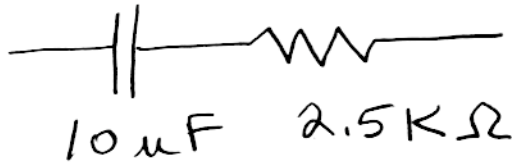- ④ write an expression for the complex impedance of the circuit branch below as a function of frequency ω . At what frequency in Hz is the phase of the impedance -45° ?



answer: 6.37 Hz

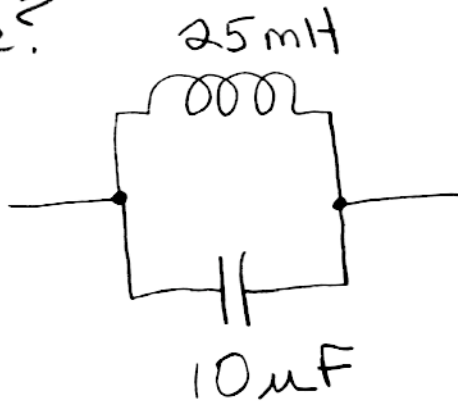- ⑤ write an expression for the complex impedance of the circuit branch below as a function of frequency ω . At what frequency in Hz is the magnitude of the impedance infinite?



answer: 318 Hz

- ⑥ what is the magnitude of the impedance in question 5 at 0 Hz? at ∞ Hz?

answer: 0, 0