

# BioE 1310 - Homework 7


① The primary of a transformer sees 120 VAC  $R_{ms}$  and has 300 turns of wire. The secondary has 50 turns. What is the peak AC voltage across the secondary? \_\_\_\_\_

answer

② The "truth table" and diode circuit for an AND gate are shown below.


A	B	A AND B	VOLTAGE AT (X)
0	0	0	—
0	1	0	—
1	0	0	—
1	1	1	—

} Fill in answers

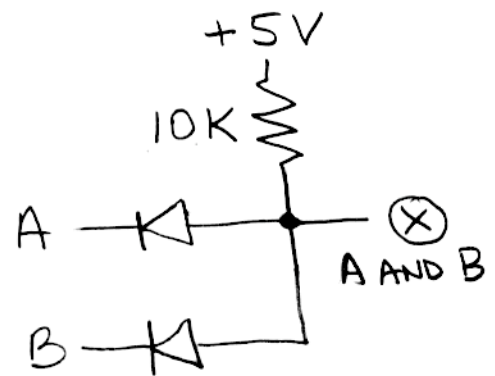

Assuming "1" means +5V and "0" means 0V, and assuming a 0.5V forward bias voltage drop across the diodes, fill in the voltage you would see at (X) for all four states

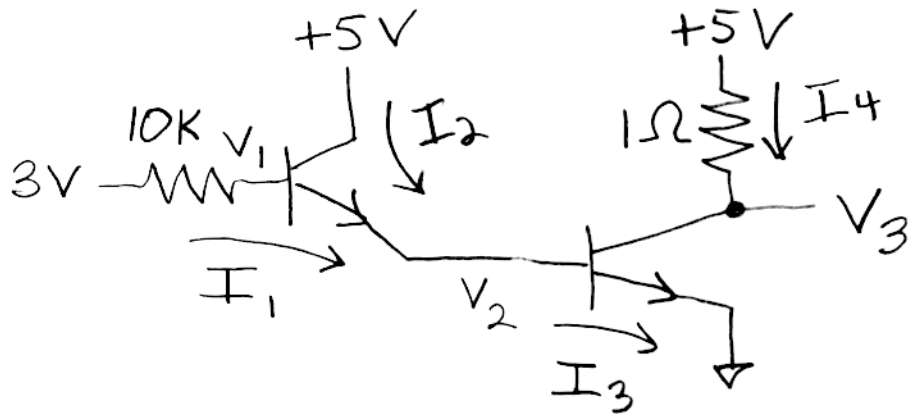
③ assuming a 0.5V forward bias voltage drop across B-E junctions, and  $\beta = 100$ , solve for the indicated voltages and currents



- $V_2$  \_\_\_\_\_
- $V_1$  \_\_\_\_\_
- $I_1$  \_\_\_\_\_
- $I_2$  \_\_\_\_\_
- $I_3$  \_\_\_\_\_
- $I_4$  \_\_\_\_\_
- $V_3$  \_\_\_\_\_

④ Do the same as in ③ for this circuit when  $V_{in} = 1.0V$  & when  $V_{in} = 1.1V$ .

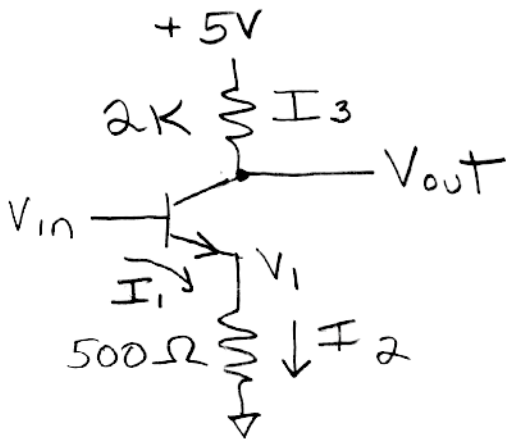What is the AC gain,  $\frac{\Delta V_{out}}{\Delta V_{in}}$ ? \_\_\_\_\_  $\leftarrow$  AC gain



- |                 |                 |
|-----------------|-----------------|
| $V_{in} = 1.0V$ | $V_{in} = 1.1V$ |
| $V_1$ _____     | $V_1$ _____     |
| $I_2$ _____     | $I_2$ _____     |
| $I_1$ _____     | $I_1$ _____     |
| $I_3$ _____     | $I_3$ _____     |
| $V_{out}$ _____ | $V_{out}$ _____ |